

TP1

Cheby

$$\omega_C = 3000\pi \quad \omega_S = 9000\pi$$

$$\alpha_{\max} = 0,5 \text{ dB} \quad \alpha_{\min} = 1,6 \text{ dB}$$

$$2\omega = 3000\pi$$

$$\omega_S = 3$$

$$\omega_C = 1$$

$$\xi^2 = 10 \frac{0,5}{10} - 1 \approx 0,122$$

$$\alpha_{\min} = 10 \log(1 + \xi^2 \cdot \cosh^{-2}(n \cdot \cosh^{-1}(\omega_S)))$$

$$n=1 \rightarrow 3,22 \text{ dB}$$

$$n=2 \rightarrow 15,59 \text{ dB}$$

$$n=3 \rightarrow 30,78 \text{ dB}$$

$n=3$

$$C_3(\omega) = 2\omega \cdot C_{n-1}(\omega) - C_{n-2}(\omega)$$

$$\downarrow \quad 2\omega \cdot (2\omega^2 - 1) - \omega$$

$$C_3(\omega) = 4\omega^3 - 3\omega$$

entonces

$$\frac{1}{1 + \xi^2 \cdot C_3(\omega)^2} = \frac{1}{1 + \xi^2 \cdot (16\omega^6 - 24\omega^4 + 9\omega^2)} = \frac{1}{\omega^6 - \frac{3}{2}\omega^4 + \frac{9}{16}\omega^2 + \frac{1}{16\xi^2}}$$

Pasando a dominio S

$$|T(s)|^2 = |T(j\omega)|^2 \Big|_{\omega=\frac{s}{j}} = \frac{\frac{1}{16\xi^2}}{\frac{s^6}{j^6} - \frac{3}{2} \cdot \frac{s^4}{j^4} + \frac{9}{16} \cdot \frac{s^2}{j^2} + \frac{1}{16\xi^2}}$$

$j^6 = -1$   
 $j^4 = 1$   
 $j^2 = -1$

$$|T(s)|^2 = \frac{\frac{1}{16\xi^2}}{-s^6 - \frac{3}{2}s^4 - \frac{9}{16}s^2 + \frac{1}{16\xi^2}}$$

Esto se implementaría con un 2do orden y 1er orden

$$T(s) = k \cdot \frac{A}{s+A} \cdot \frac{C}{s^2 + Bs + C}$$

Formando en conjunto un 3er orden

$$T(s) = D \cdot \frac{G}{s^3 + s^2 E + s F + G}$$

entonces

$$T(s) \cdot T(-s) = \frac{D \cdot G}{-s^3 + s^2 E - s F + G} \cdot \frac{D \cdot G}{s^3 + s^2 E + s F + G}$$

$$T(s) \cdot T(-s) = \frac{D^2 \cdot G^2}{-s^6 - s^4 F \cdot 2 + s^4 E^2 + 2 \cdot s^2 E G - s^2 F^2 + G^2}$$

$$T(s) \cdot T(-s) = \frac{D^2 \cdot G^2}{s^6 \cdot (-1) + s^4 \cdot (E^2 - 2F) + s^2 (2 \cdot E \cdot G - F^2) + G^2}$$

I igualando a expresión de Cheby

$$\frac{D^2 \cdot G^2}{s^6 \cdot (-1) + s^4 \cdot (E^2 - 2F) + s^2 (2 \cdot E \cdot G - F^2) + G^2} = \frac{\frac{1}{16\xi^2}}{s^6 \cdot (-1) + s^4 \cdot \left(-\frac{3}{2}\right) + s^2 \cdot \left(-\frac{9}{16}\right) + \frac{1}{16\xi^2}}$$

$$\begin{cases} G^2 = \frac{1}{16\xi^2}, D^2 = 1 \\ E^2 - 2F = -\frac{3}{2} \text{ (I)} \end{cases}$$

$$2EG - F^2 = -\frac{9}{16} \text{ (II)}$$

$$\text{(I)} \left(E^2 + \frac{3}{2}\right) \frac{1}{2} = F \rightarrow F^2 = \left(\frac{E^2}{2} + \frac{3}{4}\right)^2$$

$$\text{(II)} \quad F^2 = \frac{E^4}{4} + \cancel{2} \frac{E^2}{2} \cdot \frac{3}{4} + \frac{9}{16}$$

$$2 \cdot E \cdot G - \frac{E^4}{4} - E^2 \cdot \frac{3}{4} \cdot \frac{9}{16} = -\frac{9}{16}$$

$$E^4 \left(-\frac{1}{4}\right) + E^2 \left(-\frac{3}{4}\right) + 2 \cdot E \cdot \frac{1}{4\xi} = 0$$

$$E^3 \left(-\frac{1}{4}\right) + E \left(-\frac{3}{4}\right) + \frac{1}{2\xi} = 0 \quad (\text{con calc})$$

$$E_1 = \underline{11252912973}$$

$$E_2 > \text{conv.}$$

$$E_3$$

$$F = \underline{1,534895459}$$

con estos valores, factorizo para hallar los 2 filtros Zdo y 1er orden a utilizar

$$T(s) = K \cdot \frac{A}{s+A} \cdot \frac{C}{s^2 + BS + C} = \frac{K \cdot A \cdot C}{s^3 + BS^2 + CS + S^2 A + BAS + CA}$$

$$T(s) = \frac{K \cdot A \cdot C}{s^3 + S^2(B+A) + S(AB+C) + AC} = \frac{G}{s^3 + S^2 E + SF + G}$$

$$\left\{ \begin{array}{l} A \cdot C = G \text{ } \textcircled{I}, \quad k=1 \\ B+A = E \text{ } \textcircled{II} \\ AB+C = F \text{ } \textcircled{III} \end{array} \right.$$
$$\textcircled{I} C = \frac{G}{A}$$
$$\textcircled{II} B = E - A$$
$$A \cdot (E-A) + \frac{G}{A} = F$$

$$-A^2 + EA + \frac{G}{A} = F \quad -A^3 + EA^2 - F \cdot A + G = 0$$

con G, F y E en calculo...

$$A_1 = 0,6264564863$$

$$A_2 \text{ y } A_3 \notin$$

$$B = 0,6264564863 \quad B = A$$


$$C = 1,142449729$$

Finalmente, se llega a...

$$T_{(s)} = \frac{0,6264565}{s + 0,6264565} \cdot \frac{1,14245}{s^2 + s \cdot 0,6264565 + 1,14245}$$

$$T_{(s)} = \frac{0,71569}{s^3 + s^2 \cdot 1,252913 + s \cdot 1,5349 + 0,71569}$$

Un circuito posible podría ser

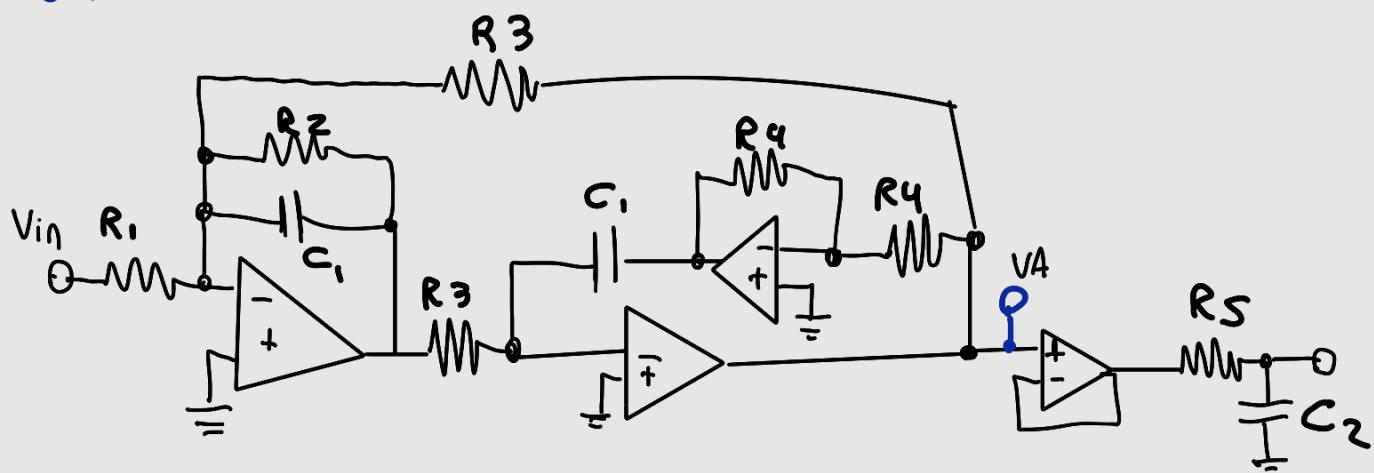

Donde  $\frac{V_2}{V_{in}}$  se podía obtener como:

$$\frac{V_{2(s)}}{V_{in(s)}} = T_{1(s)} = -\frac{G_1}{G_3} \cdot \frac{\left(\frac{G_3}{G_1}\right)^2}{s^2 + s \cdot \frac{G_2}{C_1} + \left(\frac{G_3}{G_1}\right)^2}, \quad K_1 = -\frac{G_1}{G_3}$$

$$\omega_0 = \frac{G_3}{C_1}, \quad Q_1 = \frac{G_3}{G_2}$$

Dejamos todo en función de  $C_1$

$$\textcircled{I} \quad \omega_0 \cdot C_1' = G_3' \quad \textcircled{II} \quad G_2' = \frac{\omega_0 \cdot C_1'}{Q_1} \quad \textcircled{III} \quad -G_1' = K_1 \cdot \omega_0 \cdot C_1'$$

NOTA: TOMAMOS  
 $K_1 = k_2 = -1$  para  
que entre sí se anulen

Por el lado de  $T_{2(s)}$  ..

$$\frac{V_o}{V_a} = T_{2(s)} = \frac{\frac{1}{R_s C_2}}{s + \frac{1}{R_s C_2 \omega_0}} = \frac{0,6264565}{s + 0,6264565}$$

donde

$$G_5' = \omega_0 \cdot C_2' \quad \text{IV}$$

PARA DESNORMALIZAR, sé que

$$\omega_0 = 3000\pi$$

$$\text{ELIGO } C_1 \text{ y } C_2 \text{ UTILIZABO...} \quad C_1 = C_2 = 100\text{nF}$$

DESNORMALIZO  $\omega_0$

$$T_{1(s)} = \frac{1,14245}{s^2 + s \cdot 0,6264565 + 1,14245}$$

$$\rightarrow T_{1(s)} = \frac{101,48 \cdot 10^6}{s^2 + s \cdot 5,904 \cdot 10^3 + 101,48 \cdot 10^6}$$

$$T_{2(s)} = \frac{s \cdot 5,904 \cdot 10^3}{s + s \cdot 5,904 \cdot 10^3}$$

Retomando ecuaciones ① - ⑦.

$$G_3 = \sqrt{101,48 \cdot 10^6} \cdot 100\text{nF} = 1,007 \cdot 10^3 \rightarrow R_3 = 992,68\Omega$$

$$G_2 = 5,904 \cdot 10^3 \cdot 100\text{nF} : 590412 \cdot 10^6 \rightarrow R_2 = 1,68\text{k}\Omega$$

$$G_1 = k \cdot G_3 = G_3 \rightarrow R_1 = 992,68$$

$$G_4 = G_1$$

$$R_4 = 992,68$$

$$G_5 = 5,904 \cdot 100\text{nF} \rightarrow R_5 = 169\Omega$$

con  $R_2$  y  $R_S$  tendriamos un error  $\approx 10\%$ .

Probamos otros valores de  $C_1$  y  $C_2$ .

$$C_1 = C_2 = 5,6 \text{ nF}$$

$$R_1 = R_3 = R_S = 17,72 \text{ k}\Omega$$

$$R_2 = R_5 = 30,17 \text{ k}\Omega$$

$$R_{1n} = R_{3n} = R_{5n} = 18 \text{ k}\Omega$$

$$R_2n = R_5n = 33 \text{ k}\Omega$$