

αmáx [dB]	ωp [r/s]	ωs [r/s]
1	1	2,5

1. Obtener la función transferencia T(s) de Bessel para N: 2, 3 y 4 normalizados para  $D(\omega = 0) = 1s$  utilizando el método de Storch:  
ver Schaumann, R. - Van Valkenburg, Mac E., Design of Analog Filters, Capítulo 10: Delay Filters. Sección 10.2: Bessel-Thomson Response. Página 403.

N=2

$$\cotgh \approx \frac{1}{s} + \frac{1}{\frac{3}{s}} = \frac{3+s^2}{3s} \rightarrow B_2 = s^2 + 3s + 3$$

$$\underline{T_2(s)} = \frac{B_2(0)}{B_2(s)} = \frac{3}{s^2 + 3s + 3}$$

N=3

$$\cotgh \approx \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{1}{\frac{5}{s}}} = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{s}{5}} = \frac{1}{s} + \frac{5s}{15+s^2} = \frac{5s^2+15+s^2}{s^3+15s}$$

$$B_3 = s^3 + 6s^2 + 15s + 15$$

$$\underline{T_3(s)} = \frac{15}{s^3 + 6s^2 + 15s + 15}$$

N=4

$$B_4 = (2 \cdot 4 - 1) \cdot B_3 + s^2 B_2 = 7 \cdot (s^3 + 6s^2 + 15s + 15) + s^2 \cdot (s^2 + 3s + 3)$$

$$= 7s^3 + 42s^2 + 105s + 105 + s^4 + 3s^3 + 3s^2 = s^4 + 10s^3 + 45s^2 + 105s + 105$$

$$T_{4(5)} = \frac{105}{s^4 + 10s^3 + 45s^2 + 105s + 105}$$

2. Elegir la  $T(s)$  con el mínimo orden que cumpla con  $\alpha_{\max} = 1dB$ .

$$N = 2$$

$$T_2(\omega) = \frac{3}{-\omega^2 + 3j\omega + 3} = \frac{3}{3\omega^2 + j3\omega}$$

$$|T_2(\omega)| = \frac{3}{\sqrt{(3-\omega^2)^2 + (3\omega)^2}} = \frac{3}{\sqrt{9 - 6\omega^2 + \omega^4 + 9\omega^2}} = \frac{3}{\sqrt{\omega^4 + 3\omega^2 + 9}}$$

$$|\chi_{2(\omega_p=1)}| = \left( \frac{3}{\sqrt{1+3+9}} \right)^{-1} = \frac{\sqrt{13}}{3} \approx 1.2$$

$$\underline{\chi_{2(\omega_p=1)}}_{dB} = 10 \log \left( \frac{\sqrt{13}}{3} \right) \approx 0.7985 \text{ dB}$$
Cumple

$$N=3$$

$$T_3(\omega) = \frac{15}{-j\omega^3 - 6\omega^2 + 15j\omega + 15} = \frac{15}{-6\omega^2 + 15 + j(-\omega^3 + 15\omega)}$$

$$|T_3(\omega)| = \frac{15}{\sqrt{(15-6\omega^2)^2 + (15\omega-\omega^3)^2}}$$

$$|\chi_{3(\omega_p=1)}| = \frac{15}{\sqrt{(15-6)^2 + (15-0)^2}} \approx 0.901$$

$$\underline{\chi_{(\omega_p=1)}}_{dB} = -10 \log \left( \frac{15}{\sqrt{81+180}} \right) = 0.451 \text{ dB}$$

$$N = 4$$

$$T_4(\omega) = \frac{105}{\omega^4 - j\omega^3 10 - 4s\omega^2 + j\omega 10s + 105}$$

$$|T_4(\omega)| = \frac{105}{\sqrt{(\omega^4 - 4s\omega^2 + 105)^2 + (-\omega^3 10 + \omega 105)^2}}$$

$$|T_4(\omega_p=1)| = \frac{105}{\sqrt{(1-4s+105)^2 + (-10+105)^2}} = \frac{105}{\sqrt{12746}} \approx 0.83$$

$$\underline{\alpha_q(\omega_p=1)}_{dB} = 10 \cdot \log \left( \frac{\sqrt{12746}}{105} \right) \approx 0.315 dB$$

CON  $n=2$  YA CUMPLE ...

3. Evaluar el retardo de grupo  $D(\omega = 2.5)$  y expresar en forma porcentual [%] el error o desviamiento respecto a  $D(\omega = 0)$ .

$$D(\omega) = -\frac{\partial \angle T(\omega)}{\partial \omega} \quad \angle T_2(\omega) = -\tan^{-1} \left( \frac{3\omega}{3-\omega^2} \right)$$

$$D(\omega) = \frac{1}{1 + \frac{3\omega}{3-\omega^2}} \cdot \left[ \frac{3 \cdot (3-\omega^2) - (-2\omega) \cdot 3\omega}{(3-\omega^2)^2} \right]$$

$$D(\omega) = \frac{3-\omega^2}{-\omega^2+3\omega+3} \cdot \frac{9+3\omega^2}{(3-\omega^2)^2}$$


$$D_{(\omega=0)} = \frac{3 \cdot \frac{Q}{Q}}{3 \cdot 3^2} = \underline{\underline{1}} \quad \text{Se cumple}$$

$$D_{(\omega=2\omega_s)} = \frac{(3 - \frac{25}{4})(9 + 3 \cdot \frac{25}{4})}{(-\frac{25}{4} + 3 \cdot \frac{5}{2} + 3)(3 - \frac{25}{4})^2} = \frac{-1443/16}{2873/64} \approx \underline{\underline{-2}}$$

En  $D_{(\omega=2\omega_s)}$ , el  $E_{\%}$  es del -100%.

$$E_{\%} = \frac{D_{(0)} - D_{(2\omega_s)}}{D_{(0)}} \cdot 100\% = \frac{1-2}{1} \cdot 100\% = -100\%$$

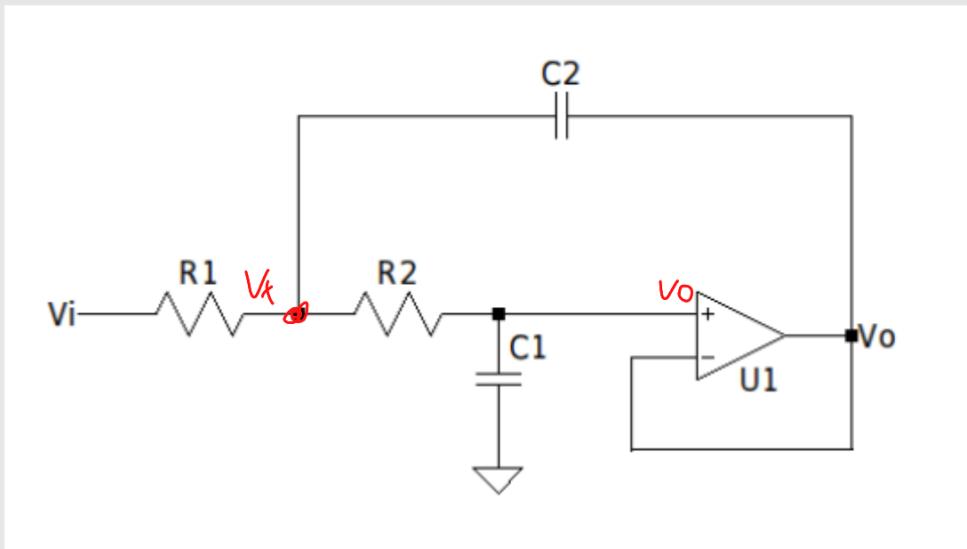4. Sintetizar el circuito **NORMALIZADO** con estructuras Sallen-Key con  $K=1$  (real, negativa y unitaria).



$$V_x(G_1 + G_2 + 5C_2) - V_i(G_1) - V_o(G_2 + 5C_2) = 0$$

$$V_o(G_2 + 5C_1) - V_x(G_2) = 0$$

$$V_x = V_o \left( \frac{5C_1}{G_2} + 1 \right)$$

$$V_o \cdot \left( \frac{5C_1}{G_2} \cdot G_1 + 5C_1 + 5 \frac{C_1 C_2}{G_2} + G_1 \cdot G_2 + 5C_2 - 5G_2 - G_2 \right) = V_i(G_1)$$

$$\frac{V_o}{V_i} = \frac{G_1}{S^2 C_1 C_2 + S \cdot C_1 \left( \frac{G_1}{G_2} + 1 \right) + G_1} = \frac{G_2 \cdot G_1 / C_1 C_2}{S^2 + S \cdot \frac{1}{C_2} \cdot (G_1 + G_2) + G_1 G_2 / C_1 C_2}$$

$$T_{(S)} = \frac{\frac{G_1 \cdot G_2}{C_1 \cdot C_2}}{S^2 + S \cdot \frac{G_1 + G_2}{C_2} + \frac{G_1 G_2}{C_1 \cdot C_2}}$$

$$\omega_0 = \sqrt{\frac{G_1 G_2}{C_1 C_2}} \quad Q = \frac{\sqrt{\frac{G_1 G_2}{C_1 C_2}}}{\frac{G_1 + G_2}{C_2}} \rightarrow Q = \frac{\sqrt{G_1 \cdot G_2 \cdot \frac{C_2}{C_1}}}{G_1 + G_2}$$

NO tomo ninguna SIMPLIFICACIÓN pq me limito  $Q \geq \text{un valor fijo}$

y antes..

$$T_2(S) = \frac{3}{S^2 + 3S + 3} \quad \omega_0 = \sqrt{3}, \quad Q = \frac{\sqrt{3}}{3}$$

entonces

$$\textcircled{I} \quad 3 = \frac{G_1 G_2}{C_1 C_2}, \quad \frac{\sqrt{3}}{3} \cdot \frac{\sqrt{3}}{\frac{G_1 + G_2}{C_2}} \textcircled{II} \quad Q$$

$$\textcircled{III} \quad 3 = \frac{G_1 + G_2}{C_2} \quad \text{y} \quad \textcircled{IV} \quad 3 = \frac{G_1 \cdot G_2}{C_1 \cdot C_2} \quad \textcircled{I}$$

$$\frac{3}{3} \cdot \frac{(G_1 + G_2) / C_2}{G_1 \cdot G_2 / C_1 \cdot C_2} = 1 = \frac{(G_1 + G_2) C_1}{G_1 G_2} \quad \frac{1}{C_1} = G_1 // G_2$$

$$C_1 = 1, G_1 = G_2 = 2 \rightarrow C_2 = \frac{4}{3}$$

COMPROUEBO

$$T(s) = \frac{\frac{G_1 \cdot G_2}{C_1 \cdot C_2}}{s^2 + s \cdot \frac{G_1 + G_2}{C_2} + \frac{G_1 G_2}{C_1 \cdot C_2}} = \frac{3}{s^2 + s \cdot 3 + 3}$$

$$\left| \begin{array}{l} G_1 = 2 \\ G_2 = 2 \\ C_1 = 1 \\ C_2 = \frac{4}{3} \end{array} \right.$$

- +10 💎 DESNORMALIZAR los componentes para obtener un  $D(\omega = 0) = 200\mu s$ .

Recálculo  $D(\omega)$  en función de  $\omega_0$  y  $Q$

$$T(s) = \frac{\omega_0^2}{s^2 + s \cdot \frac{\omega_0}{Q} + \omega_0^2} \rightarrow T(\omega) = \frac{\omega_0^2}{j\omega \frac{\omega_0}{Q} + \omega_0^2 - \omega^2}$$

$$T(\omega) = -j \frac{\omega \cdot \omega_0 / Q}{\omega_0^2 - \omega^2}$$

$$D(\omega) = \frac{1}{1 + \frac{\omega_0 \cdot \omega / Q}{\omega_0^2 - \omega^2}} \cdot \frac{\omega_0 / Q \cdot (\omega_0^2 - \omega^2) + \omega \cdot \omega_0 / Q \cdot 2\omega}{(\omega_0^2 - \omega^2)^2}$$

$$\omega' = \frac{\omega_0}{\omega}$$

DESNORMALIZO

$$\omega' = \frac{\omega}{\omega_0}$$

$$D(\omega) = \frac{1}{1 + \frac{\omega_0 \cdot \omega \cdot \Omega \omega^2 / \alpha}{\Omega \omega^2 (\omega_0^2 - \omega^2)}} \cdot \frac{\Omega \omega^3 \cdot \frac{\omega_0}{\alpha} (\omega_0^2 - \omega^2) + \Omega \omega^3 \frac{2\omega^2 \cdot \omega b}{\alpha}}{\Omega \omega^4 (\omega_0^2 - \omega^2)^2}$$

Reemplazo con  $\omega=0$

$$D(0) = \frac{1}{1 + \frac{0}{\Omega \omega^2 \cdot \omega_0^2}} \cdot \Omega \omega^3 \cdot \frac{\frac{\omega_0^3}{\alpha} + 0}{\Omega \omega^4 \cdot \omega_0^4}$$

$\omega_0 = \sqrt{3}$   
 $\alpha = \frac{\sqrt{3}}{3}$   
 $\frac{\omega_0}{\alpha} = 3$

$$D(0) = 1 \cdot \Omega \omega^3 \cdot \frac{\cancel{\alpha}}{\cancel{\Omega \omega^4 \cdot \alpha}}$$

$$D(0) = \frac{1}{\Omega \omega} = 200 \mu S$$

$$\Omega \omega = (200 \cdot 10^{-6} s)^{-1}$$

$$\boxed{\Omega \omega = 5 \cdot 10^3}$$