

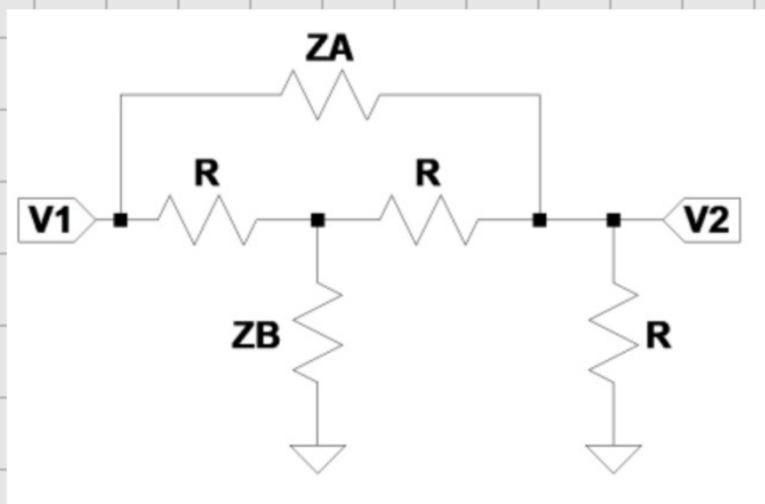


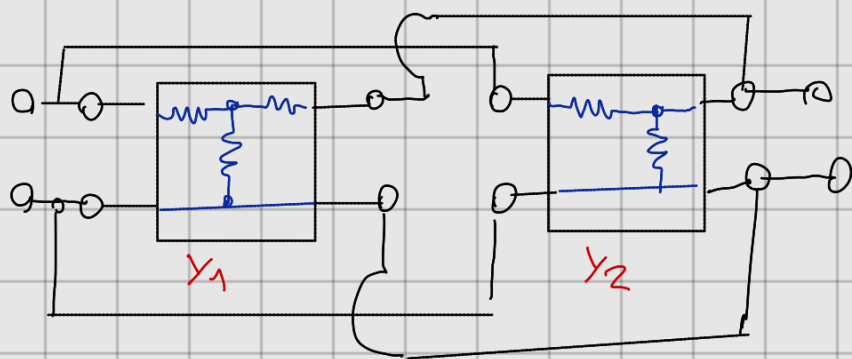

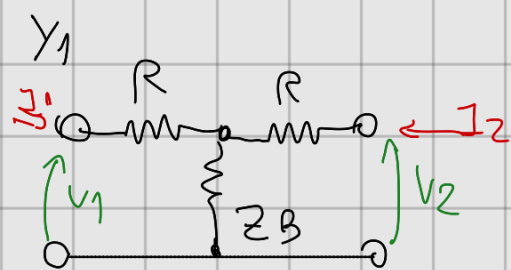Se puede dividir en 2 cuadripolos, uno de ellos tee.



como están en paralelo, trabajo con parámetros ADMITANCIA



$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = (G + Y_B) \parallel G$$

$$Y_{11}$$

$$= \frac{\frac{R+Z_B}{R \cdot Z_B} \cdot \frac{1}{R}}{\frac{1}{R} + \frac{R+Z_B}{R \cdot Z_B}}$$

$$\boxed{Y_{11} = \frac{\frac{R+Z_B}{R \cdot Z_B}}{\frac{Z_B + R + Z_B}{R \cdot Z_B}} = \frac{R+Z_B}{(R+2Z_B) \cdot R}}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$



$$I_1 \Big|_{V_1=0} = V_2 \cdot \frac{R // Z_B}{R // Z_B + R} \cdot \frac{1}{R} \cdot (-1)$$

$$Y_{12} = -\frac{1}{R} \cdot \frac{\frac{R \cdot Z_B}{R + Z_B}}{\frac{R \cdot Z_B}{R + Z_B} + R} = -\frac{1}{R} \cdot \frac{R \cdot Z_B}{2R \cdot Z_B + R^2} = -\frac{Z_B}{2R \cdot Z_B + R^2}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$



$$I_2 \Big|_{V_2=0} = V_1 \cdot \frac{R // Z_B}{R // Z_B + R} \cdot \frac{1}{R} \cdot (-1) \quad \text{idem } Y_{12}..$$

$$Y_{21} = Y_{12}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$



$$Y_{22} = \left(R // Z_B + R \right)^{-1}$$

$$Y_{22} = \left(\frac{R \cdot Z_B}{R + Z_B} + R \right)^{-1} = \left(\frac{R \cdot Z_B + R^2 + R \cdot Z_B}{R + Z_B} \right)^{-1} = \frac{R + Z_B}{R^2 + 2R \cdot Z_B}$$

$$Y_1 = \begin{pmatrix} \frac{R + Z_B}{R(R + 2Z_B)} & -\frac{Z_B}{R(R + 2Z_B)} \\ -\frac{Z_B}{R(R + 2Z_B)} & \frac{R + Z_B}{R(R + 2Z_B)} \end{pmatrix}$$

luego, Y_2 .




$$Y_{21} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{Z_A}$$

$$Y_{21} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{Z_A}$$



$$Y_{22} = \frac{I_2}{V_1} \Big|_{V_2=0} = -\frac{1}{Z_A}$$

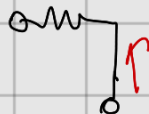

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{Z_A} + \frac{1}{R} = \frac{Z_A + R}{Z_A \cdot R}$$

Entonces

$$Y_2 = \begin{bmatrix} 1/Z_A & -1/Z_A \\ -1/Z_A & (Z_A + R)/Z_A \cdot R \end{bmatrix}$$

FINALMENTE, Y_{TOTAL} .

$$Y_{TOT} = Y_1 + Y_2$$

$$Y_{TOT} = \frac{1}{R(R+Z_B)} \cdot \begin{bmatrix} R+Z_B & -Z_B \\ -Z_B & R+Z_B \end{bmatrix} + \frac{1}{Z_A} \begin{bmatrix} 1 & -1 \\ -1 & \frac{Z_A+R}{R} \end{bmatrix}$$

$$R \cdot Z_A + \cancel{Z_A Z_B} - \cancel{Z_A R} + \cancel{Z_A Z_B} + R^2 + R \cdot Z_B$$

$$Y_{TOT} = \frac{1}{Z_A \cdot R \cdot (R + 2Z_B)} \cdot \begin{pmatrix} Z_A \cdot (R + Z_B) + R(R + 2Z_B) & -Z_B \cdot Z_A - R(R + 2Z_B) \\ -Z_B Z_A - R(R + 2Z_B) & (R + Z_B)Z_A + (Z_A + R)(R + Z_B) \end{pmatrix}$$

$$Y_{TOT} = \frac{1}{Z_A \cdot R \cdot (R + 2Z_B)} \begin{pmatrix} R \cdot (R + 2Z_B + Z_A) + Z_A Z_B & -R(R + 2Z_B) - Z_A Z_B \\ -R \cdot (R + 2Z_B) - Z_A Z_B & 3 \cdot Z_A Z_B + R \cdot (R + 2Z_A + 2Z_B) \end{pmatrix}$$

CON $Z_A = \frac{R}{Z_B}$

$$Y_{TOT} = \frac{1}{\frac{R^3}{Z_B} + 2R^2} \cdot \begin{pmatrix} R \cdot (R + 2Z_B + \frac{1}{Z_B} + 1) & -R \cdot (R + 2 \cdot Z_B + 1) \\ -R(R + 2 \cdot Z_B + 1) & R \cdot (R + 2 \frac{R}{Z_B} + 2Z_B + 3) \end{pmatrix}$$

PARA COMPROBAR CON SIMULACIONES, ASIGNO $R = Z_B = 1$
(Y $Z_A = 1$)

$$Y_{TOT} = \frac{1}{3} \cdot \begin{pmatrix} 5 & -4 \\ -4 & 8 \end{pmatrix}$$

$$Y_{TOT} = \begin{pmatrix} \frac{5}{3} & -\frac{4}{3} \\ -\frac{4}{3} & \frac{8}{3} \end{pmatrix}$$